

CO502 - Part 1 (Planning)

Group 1

Table of Contents

| | |
|---------------------------------|-----------|
| Table of Contents..... | 1 |
| Activity 1..... | 2 |
| Instructions and Opcodes..... | 3 |
| Activity 2..... | 6 |
| Hardware Units and Signals..... | 7 |
| Control Unit..... | 7 |
| Register File..... | 8 |
| ALU..... | 8 |
| Branch Logic..... | 9 |
| Data Memory..... | 10 |
| Activity 3..... | 10 |
| Unit Testing..... | 10 |
| Formal Verification..... | 11 |


Activity 1

There are four core instruction formats:

- R-type - Arithmetic and load operations. All operations read the rs1 and rs2 registers as source operands and write the result into register rd. The funct7 and funct3 fields select the type of operation.
- I-type - Arithmetic, load and system operations. Reads one 12-bit immediate operand and one register operand (rs1) and writes to rd
- S-type - Store instructions transfer a value between the registers and memory.
- U-type - Upper immediate instructions. Loads a 20-bit immediate value into a register.

Further, two variants of the instruction formats exist based on the handling of immediate:

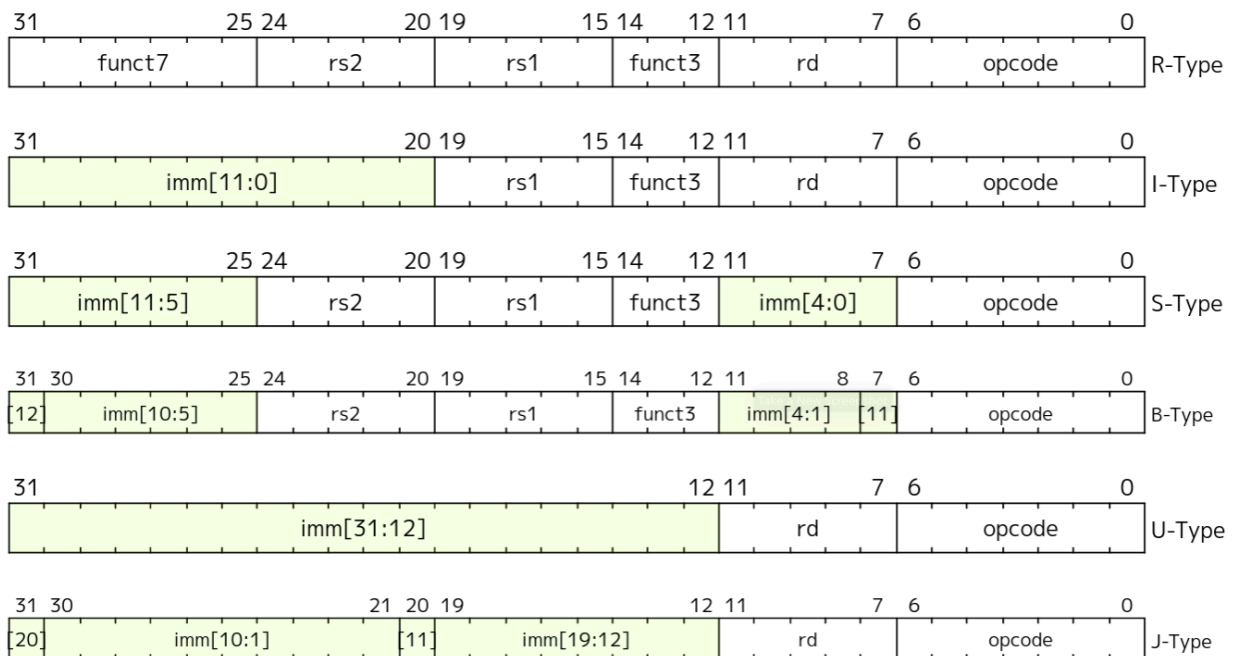- J-type - Unconditional jumps and writes return address to rd
- B-type - Conditional branching based on the comparison between values in rs1 and rs2.



Instruction Encoding Formats

Instructions and Opcodes


| Instruction | Description | Opcode | funct3 | funct7 | Notes |
|-------------|-----------------------------------|---------|--------|--------|-------------|
| R-Type | | | | | |
| ADD | $rd = rs1 + rs2$ | 0110011 | 0x0 | 0x00 | |
| SUB | $rd = rs1 - rs2$ | 0110011 | 0x0 | 0x20 | |
| XOR | $rd = rs1 \wedge rs2$ | 0110011 | 0x4 | 0x00 | |
| OR | $rd = rs1 \mid rs2$ | 0110011 | 0x6 | 0x00 | |
| AND | $rd = rs1 \& rs2$ | 0110011 | 0x7 | 0x00 | |
| SLL | $rd = rs1 \ll rs2$ | 0110011 | 0x1 | 0x00 | |
| SRL | $rd = rs1 \gg rs2$ | 0110011 | 0x5 | 0x00 | |
| SRA | $rd = rs1 \gg rs2$ | 0110011 | 0x5 | 0x20 | Sign extend |
| SLT | $rd = (rs1 < rs2) ? 1:0$ | 0110011 | 0x2 | 0x00 | |
| SLTU | $rd = (rs1 > rs2) ? 1:0$ | 0110011 | 0x3 | 0x00 | |
| MUL | $rd = (rs1 \times rs2)[31:0]$ | 0110011 | 0x0 | 0x01 | |
| MULH | $rd = (rs1 \times rs2)[63:32]$ | 0110011 | 0x1 | 0x01 | |
| MULHSU | $rd = (rs1 \times rs2)[63:32]$ | 0110011 | 0x2 | 0x01 | |
| MULHU | $rd = (rs1 \times rs2)[63:32]$ | 0110011 | 0x3 | 0x01 | |
| DIV | $rd = rs1 \div rs2$ | 0110011 | 0x4 | 0x01 | |
| DIVU | $rd = rs1 \div rs2$ (unsigned) | 0110011 | 0x5 | 0x01 | |

| | | | | | |
|--------|---------------------------------|---------|-----|----------------|-------------------------------|
| REM | rd = rs1 % rs2 | 0110011 | 0x6 | 0x01 | |
| REMU | rd = rs1 % rs2 (unsigned) | 0110011 | 0x7 | 0x01 | |
| I-Type | | | | | |
| ADDI | rd = rs1 + imm | 0010011 | 0x0 | | Imm value is sign-extended |
| XORI | rd = rs1 ^ imm | 0010011 | 0x4 | | Imm value is sign-extended |
| ORI | rd = rs1 imm | 0010011 | 0x6 | | Imm value is sign-extended |
| ANDI | rd = rs1 & imm | 0010011 | 0x7 | | Imm value is sign-extended |
| SLLI | rd = rs1 << imm[4:0] | 0010011 | 0x1 | imm[5:11]=0x00 | |
| SRLI | rd = rs1 >> imm[4:0] | 0010011 | 0x5 | imm[5:11]=0x00 | |
| SRAI | rd = rs1 >> imm[4:0] | 0010011 | 0x5 | imm[5:11]=0x20 | |
| SLTI | rd = (rs1 < imm)?1:0 | 0010011 | 0x2 | | Imm value is sign-extended |
| SLTIU | rd = (rs1 > imm)?1:0 | 0010011 | 0x3 | | Imm value is zero-extended |
| LB | rd = mem[rs1+im m][7:0] | 0000011 | 0x0 | | |
| LH | rd = mem[rs1+im m][15:0] | 0000011 | 0x1 | | |
| LW | rd = mem[rs1+im m][31:0] | 0000011 | 0x2 | | |
| LBU | rd = mem[rs1+im m][7:0] | 0000011 | 0x4 | | zero-extends |

| | | | | | |
|--------|--------------------------------|---------|-----|-----------|---------------------|
| LHU | rd = mem[rs1+imm][15:0] | 0000011 | 0x5 | | zero-extends |
| JALR | rd = PC+4; PC = rs1 + imm | 1100111 | | | |
| ECALL | Transfer control to OS | 1110011 | 0x0 | Imm = 0x0 | |
| EBREAK | Transfer control to debugger | 1110011 | 0x0 | Imm = 0x1 | |
| S-Type | | | | | |
| SB | mem[rs1+imm][7:0] = rs2[7:0] | 0100011 | 0x0 | | |
| SH | mem[rs1+imm][15:0] = rs2[15:0] | 0100011 | 0x1 | | |
| SW | mem[rs1+imm][31:0] = rs2[31:0] | 0100011 | 0x2 | | |
| SBU | | 0100011 | 0x4 | | |
| SHU | | 0100011 | 0x5 | | |
| U-Type | | | | | |
| LUI | rd = imm << 12 | 0110111 | - | | Load Upper Imm |
| AUIPC | rd = PC + (imm << 12) | 0010111 | - | | Add Upper Imm to PC |
| B-Type | | | | | |
| BEQ | if(rs1 == rs2) PC += imm | 1100011 | 0x0 | | |
| BNE | if(rs1 != rs2) PC += imm | 1100011 | 0x1 | | |
| BLT | if(rs1 < rs2) | 1100011 | 0x4 | | |

| | | | | | |
|---------|-----------------------------|---------|-----|--|--------------|
| | PC += imm | | | | |
| BGE | if(rs1 >= rs2) PC += imm | 1100011 | 0x5 | | |
| BLTU | if(rs1 < rs2) PC += imm | 1100011 | 0x6 | | zero-extends |
| BGEU | if(rs1 >= rs2) PC += imm | 1100011 | 0x7 | | zero-extends |
| J-Type | | | | | |
| JAL | rd = PC+4; PC += imm | 1101111 | - | | |
| FENCE | | 0001111 | 0x0 | | |
| FENCE.I | | 0001111 | 0x1 | | |

Activity 2

 


Pipeline Diagram with Datapath and Control

Hardware Units and Signals

Control Unit

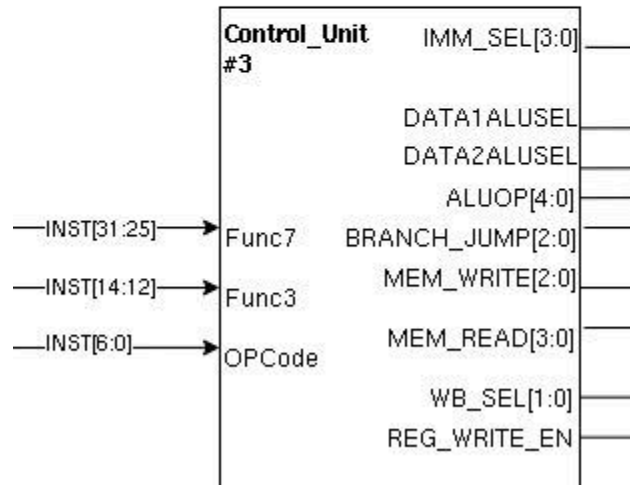The control unit interprets instruction fields and generates control signals to coordinate data flow and operations within the processor. The table below summarizes key control signals and decoding fields used for instruction execution in a RISC-V pipeline.




Control Signals and Instruction Decoding Fields

| Signal / Field | Description |
|----------------|--|
| OPCODE | Specifies the main operation to be performed; used for primary instruction decoding. |
| FUNC7 | Further decodes R-type instructions to determine the exact ALU operation. |
| FUNC3 | Distinguishes between multiple operations under the same opcode. |
| IMM_SEL | Selects the format of the immediate value (I-type, S-type, B-type, etc.). |
| DATA1_ALU_SEL | Selects the source for the first ALU operand (typically from register or PC). |
| DATA2_ALU_SEL | Selects the source for the second ALU operand (register, immediate, etc.). |
| ALU_OP | Specifies the operation that the ALU should perform (add, sub, and, or, etc.). |
| BRANCH_JUMP | Indicates if the current instruction is a branch or jump; also determines the branch type (e.g., BEQ, BNE, JAL). |
| MEM_WRITE | Enables writing data to memory. |
| MEM_READ | Enables reading data from memory. |
| WB_SEL | Selects the correct source (ALU, memory, or immediate) to write back to the register file. |
| REG_WRITE_EN | Enables writing to the register file (i.e., allows the destination register to be updated). |

Register File

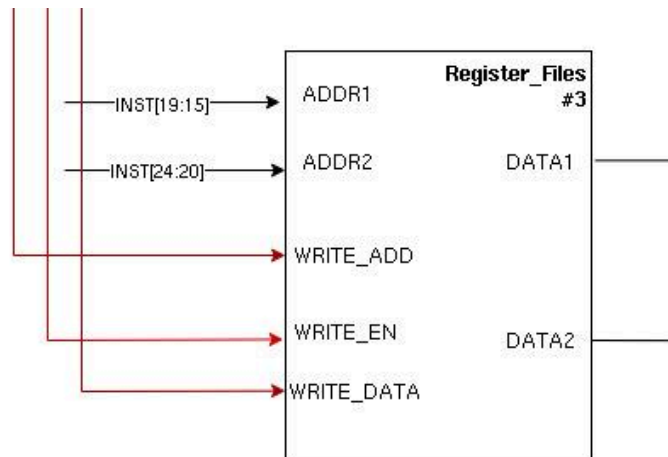The register file provides fast storage for operands and results during instruction execution. The following signals are used to control register selection, reading, and writing.



Register File Control Signals and Ports


| Signal / Port | Description |
|---------------|--|
| ADDR1 | Selects the address of the first source register for a read operation. |
| ADDR2 | Selects the address of the second source register for a read operation. |
| WRITE_ADD | Specifies the address of the destination register for a write operation. |
| WRITE_EN | Enables writing data to the selected destination register. |
| WRITE_DATA | The data value to be written into the destination register. |
| DATA1 | The data read from the register specified by ADDR1. |
| DATA2 | The data read from the register specified by ADDR2. |

ALU

The Arithmetic Logic Unit (ALU) performs arithmetic and logical operations on input operands based on control signals. The table below outlines the key signals involved in ALU operation.


Arithmetic Logic Unit (ALU) Signals

| Signal | Description |
|----------|--|
| OPERAND1 | The first input value to the ALU, typically from a register or program counter. |
| OPERAND2 | The second input value to the ALU, from a register or an immediate value. |
| ALUOP | Control signal that determines the specific operation to be performed (e.g., add, sub, and, or). |
| ALU_OUT | The output result of the ALU operation. |

 

Branch Logic

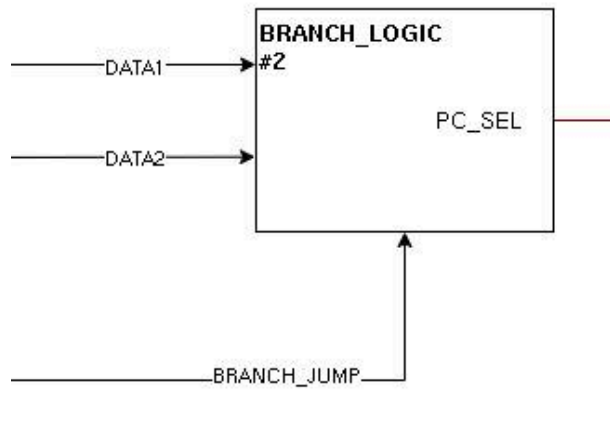The branch logic unit determines the branch taken or not taken and the next program counter (PC) value based on branch or jump conditions. It evaluates comparisons and signals the control unit to alter instruction flow when necessary.




Branch Logic Control Signals

| Signal | Description |
|-------------|--|
| BRANCH_JUMP | Indicates whether the current instruction is a branch or jump, and specifies the branch type (e.g., BEQ, JAL). |
| DATA1 | First source register value used for branch condition evaluation. |
| DATA2 | Second source register value used for branch condition evaluation. |
| PC_SEL | Control signal that selects whether to use the sequential PC or a computed branch/jump target. |

Data Memory

 The data memory module handles load and store operations during program execution. The control and data signals below manage memory access and data transfer between the processor and memory.



Data Memory Interface Signals

| Signal | Description |
|-----------|---|
| MEM_READ | Enables a memory read operation. |
| MEM_WRITE | Enables a memory write operation. |
| ADDRESS | Specifies the memory address for the read or write operation. |
| D_IN | Data to be written to memory (for store instructions). |
| D_OUT | Data read from memory (for load instructions). |

Activity 3

Unit Testing

Isolate single modules and test them using a Verilog simulator (Icarus Verilog and GTKWave) and test benches. The following factors are considered when writing the test benches:

1. Testing edge cases such as zero inputs, maximum values
2. Test units in isolation

| Unit | Expected Tests |
|--------------|---|
| Control Unit | Proper generation of control signals at correct |

| | |
|---------------|---|
| | timing |
| Register File | Proper address decoding, proper reset |
| ALU | Mathematical accuracy of operations, edge cases |
| Branch Logic | Correct PC update decisions |
| Data Memory | Proper address decoding, proper reset |

Formal Verification

Use of a framework such as RISC-V Formal (<https://github.com/YosysHQ/riscv-formal>) to formally verify the correctness of the core. The following outlines the high-level steps that need to be taken:

1. Wrap the core with the RISC-V Formal Interface (RVFI), which outputs architectural state changes (registers, PC, memory) and instruction details.
2. Use the `genchecks.py` script from `riscv-formal` to automatically generate verification properties for the core. These checks will verify that the core behaves correctly instruction-by-instruction and over sequences.
3. Run formal verification and the correctness of the core.